

Term 7- Sept 2024


Nanoelectronics and Technology
(01.119/99.503)

Week 2 Day 1 (24-Sept 2024)



Outline

- Review of MOSFETs
- CMOS Inverter circuit
- CMOS scaling


Review of MOSFETs

 

n-channel MOS
Transistor

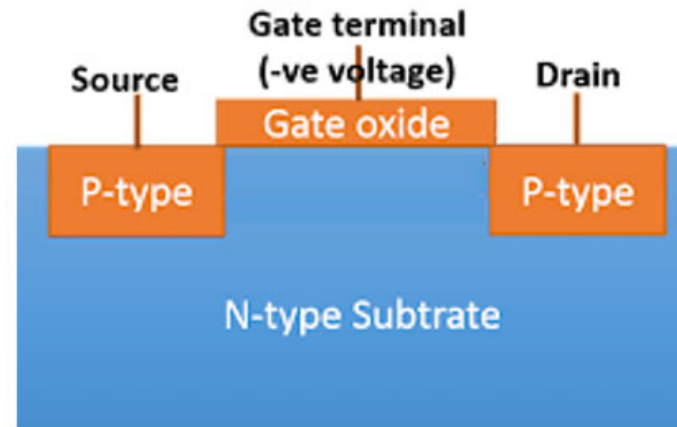 




p-channel MOS
Transistor

 

Review of MOSFETs

MOS Transistor

   - Add “source” and “drain” terminals to MOS capacitor
- Transistor types
 - NMOS: p-type substrate, n⁺ source/drain
 - PMOS: n-type substrate, p⁺ source/drain





Review of MOSFETs

What is a Transistor?


A Switch!




An MOS Transistor

  

n-channel MOS Transistor

 


p-channel MOS Transistor

 


Review of MOSFETs

Cut-off Regime

 
- MOSFET:
 - $V_{GS} < V_T$, with $V_{DS} \geq 0$
- Inversion Charge = 0
- V_{DS} drops across drain depletion region
- $I_D = 0$




n-channel MOS Transistor

 


Review of MOSFETs

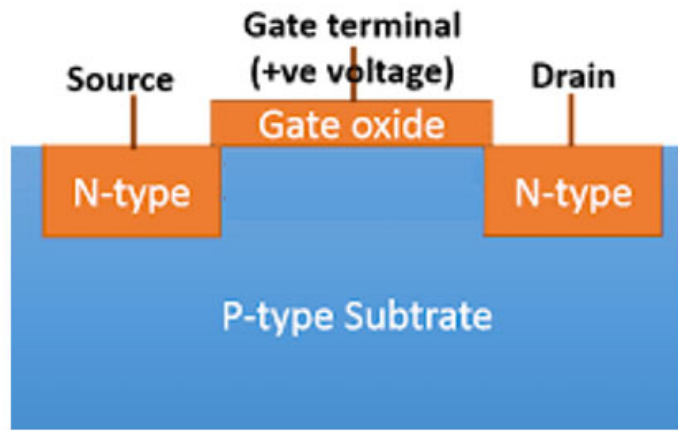

n-channel MOS Transistor

 


Linear or Triode Regime

 


$$V_{GD} = V_{GS} - V_{DS}$$

Electrons drift from source to drain \Rightarrow **electrical current!**

Review of MOSFETs


 


MOSFET Output Characteristics

 


Review of MOSFETs

$$\beta = \mu C_{ox} \frac{W}{L}$$

 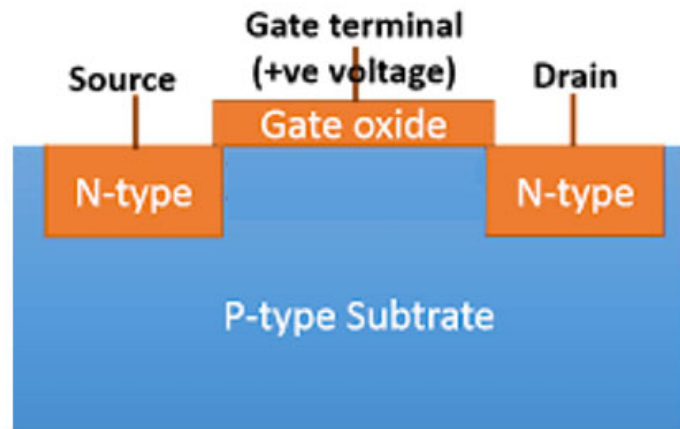


$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t & \text{cutoff} \\ \beta \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds} & V_{ds} < V_{dsat} & \text{linear} \\ \frac{\beta}{2} (V_{gs} - V_t)^2 & V_{ds} > V_{dsat} & \text{saturation} \end{cases}$$

 
Review of MOSFETs: DC load line of n-MOSFET




I_D - V_{DS} curves for various V_{GS} :

 

 Review of MOSFETs: DC load line of n-MOSFET





Load Line (Ckt Theory)




 


Review of MOSFETs

p-MOSFET

  


Review of MOSFETs

  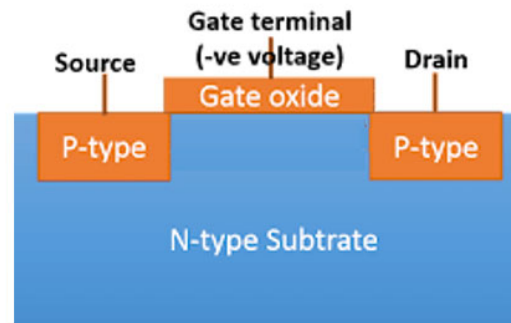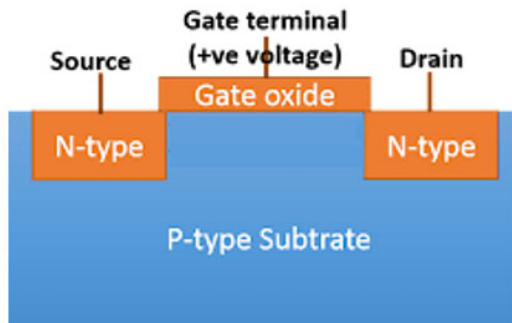


MOSFET: Threshold Voltage (V_{th})

 - The voltage needed on the Gate terminal of the MOSFET to form a thin channel beneath the gate electrode (between Source & Drain terminals).
- The current can flow between S and D terminals through the channel.
- So threshold voltage is the voltage needed to turn on the device.
- As the MOSFET is voltage controlled current source, the output current will depend on the gate voltage applied.




MOSFET: Threshold Voltage (V_{th})

 - Lower V_{th} :
 - Faster in timing
 - Higher subthreshold current
- Higher V_{th} :
 - Less leakage
 - Higher delay
- V_{th} scales with MOSFET scaling




CMOS circuit


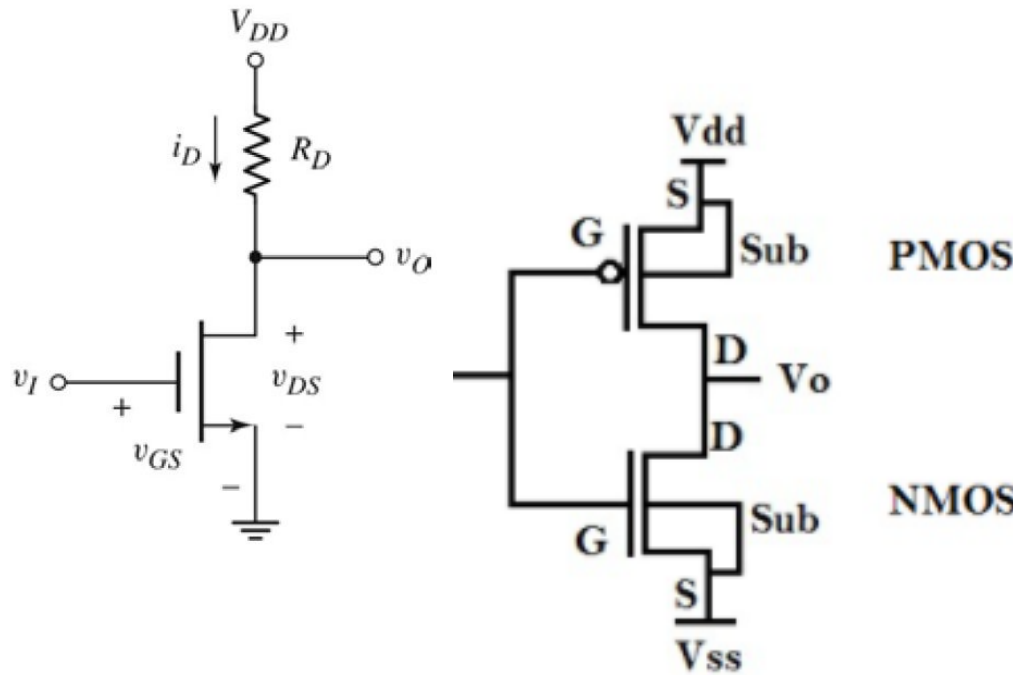


G = Gate Terminal
S = Source Terminal
D = Drain Terminal
Sub = Substrate Terminal


CMOS Inverter Operation Principle

 




CMOS circuit

  


The Ideal Inverter

 



CMOS circuit

  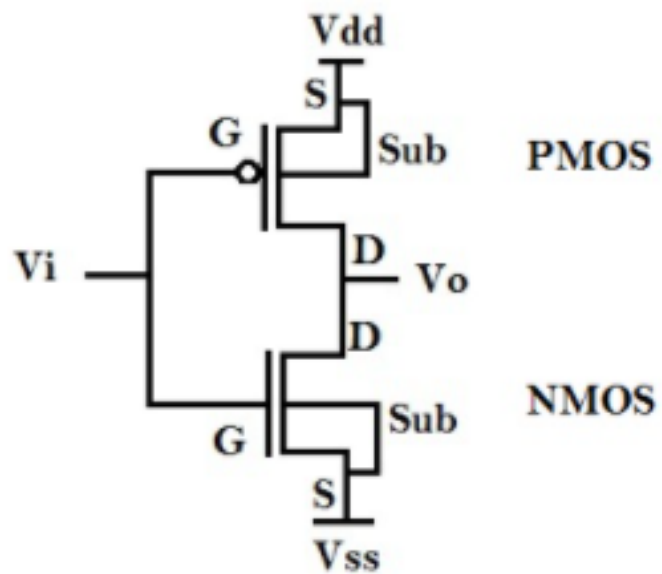



CMOS circuit

 



CMOS inverter transfer function

  

CMOS circuit

 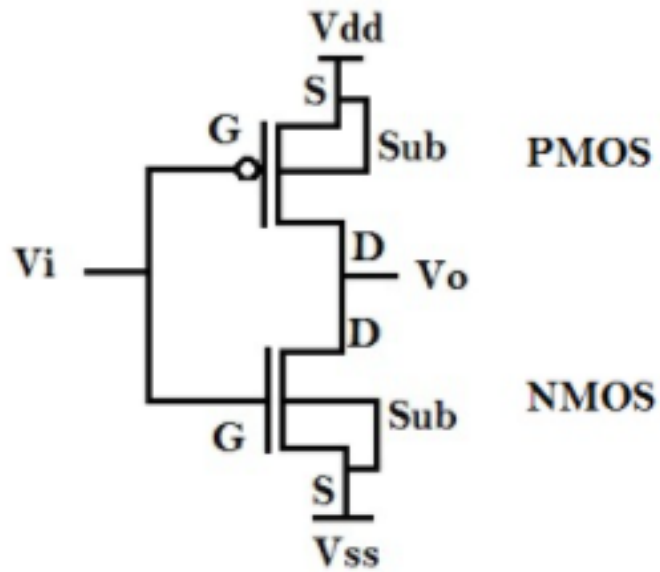

The Realistic Inverter

  

CMOS circuit: Noise Margin

- Noise margin is the ratio by which the signal exceeds the minimum acceptable amount.
- It explains up to what extent IC allows noise in the transmission of logic '0' and logic '1'.
- Logic '0' and '1' – represent the range of input values
- Hence, for error free digital signal transmission noise margin is required


CMOS circuit: Noise Margin

- Noise margin is the ratio by which the signal exceeds the minimum acceptable amount.
- It explains up to what extent IC allows noise in the transmission of logic '0' and logic '1'.
- Logic '0' and '1' – represent the range of input values
- Hence, for error free digital signal transmission noise margin is required




CMOS circuit: Noise Margin

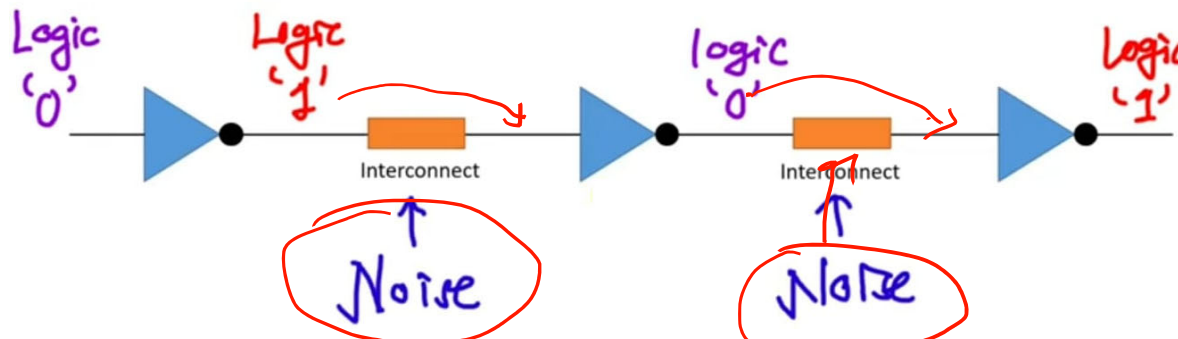- Noise margin is the ratio by which the signal exceeds the minimum acceptable amount.
- It explains up to what extent IC allows noise in the transmission of logic '0' and logic '1'.
- Logic '0' and '1' – represent the range of input values
- Hence, for error free digital signal transmission noise margin is required




CMOS circuit: Noise Margin

 


$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$

CMOS inverter transfer function

 


CMOS circuit: Noise Margin

 


$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$

CMOS circuit: Noise Margin

 

CMOS scaling: Moore's Law

 


Moore's law says that the number of transistors doubles approximately every two years.

- CMOS scaling
 - Speed
 - High density
 - Less power
 - Reduced cost/transistor

Ref: M. L. Rieger, "Retrospective on VLSI value scaling and lithography" Journal of Micro/Nanolithography-2019

CMOS scaling: Dennard's scaling

 


Dennard scaling, also known as MOSFET scaling, is a scaling law which states roughly that, as transistors get smaller, their power density stays constant, so that the power use stays in proportion with area; both voltage and current scale (downward) with length.

With feature sizes below 65nm, these rules could no longer be sustained, because of the exponential growth of the leakage current.”

Ref: M. L. Rieger, “ Retrospective on VLSI value scaling and lithography” Journal of Micro/Nanolithography-2019

CMOS scaling: Moore's Law

 

Ref: H. H. Radamson, et al., "Miniaturization of CMOS" Micromachines 10(5) 293-2019