

Term 7- Sept 2025

Nanoelectronics and Technology
(01.119/99.503)-Week 2 Class 2


Shubhakar K
25-Sept- 2025

Email: shubhakar@sutd.edu.sg
Office location: 1.602-26



Outline

- MOSFET structure
- CMOS Inverter
- CMOS Based Digital Circuits
- Noise Margin


Review of MOSFETs

 

n-channel MOS
Transistor

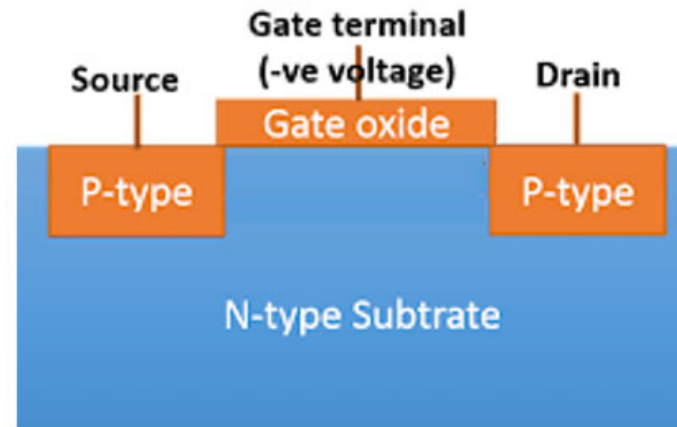 




p-channel MOS
Transistor

 

Review of MOSFETs

MOS Transistor

   
- Add “source” and “drain” terminals to MOS capacitor
- Transistor types
 - NMOS: p-type substrate, n⁺ source/drain
 - PMOS: n-type substrate, p⁺ source/drain




Review of MOSFETs

- We now turn our attention to another type of transistor, the **MOSFET**:
 - ▣ **M**etal **O**xide **S**emiconductor **F**ield **E**ffect **T**ransistor
- Many similarities to the BJT:
 - ▣ Three terminals
 - ▣ Voltage at one terminal controls current between the other two
 - A transconductance device
 - ▣ Two polarities: N-channel and P-channel MOSFETS
 - Our focus will primarily be N-channel MOSFETs (NMOS devices)



N-Channel
(NMOS):

 

P-Channel
(PMOS):

 

Review of MOSFETs

  

- P-type substrate
- N+ source and drain
- **Metal gate electrode**, and source/drain/body contacts
- Thin **oxide** insulates the gate from the rest of the device
- Region of substrate between the drain and source is the **channel**
 - Channel dimensions: W and L

Review of MOSFETs

- Terminal voltages and currents named as shown
 - ▣ Again, lower-case v/i and upper-case subscript represents **total** (AC and DC) voltage and current
- For an NMOS device in typical operation:

$$v_{GS} \geq 0$$


$$v_{DS} \geq 0$$

- Gate oxide does not allow current to flow, so

$$i_G = 0$$

and

$$i_D = i_S$$

 

Review of MOSFETs

Cut-Off Region

- Gate and source both grounded

$$v_{GS} = 0$$



- Drain-to-source pathway looks like two back-to-back diodes

- Very high drain-source resistance ($r_{DS} = \infty$)

- Even for $v_{DS} > 0$, no current will flow

$$i_D = 0$$

- Looks like an open switch

  





Review of MOSFETs

What is a Transistor?


A Switch!




An MOS Transistor

    

Review of MOSFETs

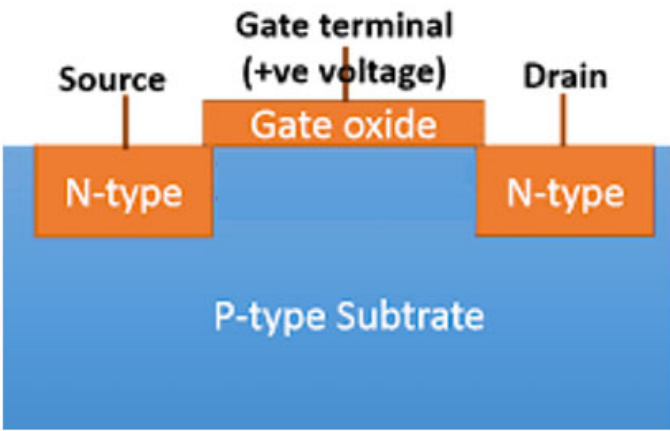


n-channel MOS
Transistor

 

Review of MOSFETs


Inversion

 

- Now, v_{GS} is increased, while v_{DS} is kept small
 - ▣ Electric field established across gate oxide
 - ▣ Holes in p-type substrate repelled deeper into substrate
 - ▣ Electrons from drain and source attracted to region below the gate
- For large enough v_{GS} , p-type material below the gate is ***inverted*** to n-type
 - ▣ An ***inversion layer***
 - ▣ ***Induced n-type channel connects drain to source***
 - ▣ Now, current can flow in response to v_{DS} , $i_D > 0$

Review of MOSFETs

Threshold Voltage

 


- Channel is induced once v_{GS} exceeds a certain voltage:
 - ▣ The **threshold voltage**

$$v_{GS} \geq V_t$$

- ▣ A device parameter
 - ▣ Typically, $V_t = 300 \text{ mV} \dots 1 \text{ V}$
- As v_{GS} increases beyond V_t , the induced channel gets deeper
- As long as v_{DS} is small ($v_{DS} \ll V_t$), channel depth is uniform

Review of MOSFETs

Overdrive Voltage

 

- A channel is induced once v_{GS} exceeds the threshold voltage
- v_{GS} in excess of the threshold voltage is called the **overdrive voltage** or **effective voltage**:

$$v_{OV} = v_{GS} - V_t$$

- As we will soon see, v_{OV} plays an important role in determining device behavior

Review of MOSFETs

Channel formation basics

- A channel forms when

$$V_{GS} > V_T$$


because inversion charge appears under the gate.

- Along the channel, the local inversion charge is

$$Q_n(x) \propto V_{GS} - V_T - V(x),$$

where $V(x)$ is the channel potential at position x .

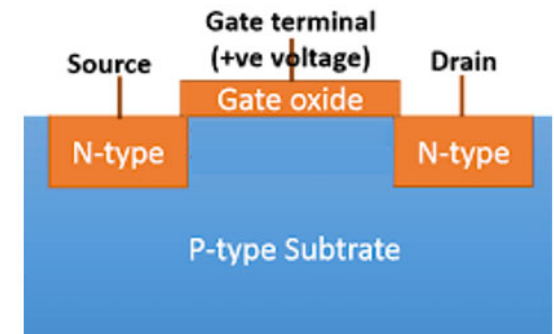- At the source end, $V(0) = 0 \implies Q_n(0) \propto V_{GS} - V_T$ (strong channel).
- At the drain end, $V(L) = V_{DS} \implies Q_n(L) \propto V_{GS} - V_T - V_{DS}$.



Review of MOSFETs

Condition for pinch-off

- If $V_{DS} < V_{GS} - V_T$:

Channel charge is positive all along the channel \rightarrow continuous inversion path from source to drain. MOSFET is in **linear/triode region**.

- If $V_{DS} = V_{GS} - V_T$:

At the **drain end**,

$$Q_n(L) = 0$$


\rightarrow the inversion channel just disappears at the drain edge \rightarrow **onset of pinch-off**.

- If $V_{DS} > V_{GS} - V_T$:


No inversion possible near the drain. Instead:

- Channel terminates at a "pinch-off point" before the drain.
- Beyond this, a depletion region carries the extra potential drop.
- Current saturates since the effective voltage across the channel is clamped at $V_{GS} - V_T$.

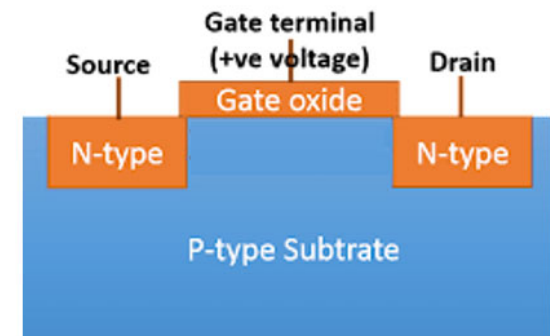
- At the source end, $V(0) = 0 \implies Q_n(0) \propto V_{GS} - V_T$ (strong channel).
- At the drain end, $V(L) = V_{DS} \implies Q_n(L) \propto V_{GS} - V_T - V_{DS}$.



Review of MOSFETs- Linear Region

 

 
- As v_{DS} increases:
 - ▣ Voltage varies along the channel
 - v_S near the source, v_D near the drain
 - ▣ Gate-to-channel voltage decreases closer to the drain
 - ▣ Channel depth decreases closer to the drain
 - Channel is tapered
- More current flows with increasing v_{DS} , but channel resistance increases as channel becomes more tapered



I
S

Review of MOSFETs- Linear Region

Channel Pinch-Off

 

- Eventually, for large enough v_{DS}
 - ▣ Gate-to-channel voltage near the drain no longer exceeds V_t
 - ▣ Channel **pinch-off** occurs
 - ▣ Channel disappears at the edge of the drain
- Pinch-off occurs when:

$$v_{GD} = V_t = v_{GS} - v_{DS}$$


$$v_{DS} = v_{GS} - V_t$$

Review of MOSFETs- Linear Region


Saturation Region

□ Once channel pinch-off occurs:

 
- Voltage at the drain-end of the channel remains v_{OV} , even as v_{DS} increases
- Any increase in v_{DS} beyond v_{OV} is dropped across the depletion region surrounding the drain
- Voltage across the length of the channel is fixed at v_{OV}
- Pinched-off channel shape does not change with v_{DS}
- Drain current **saturates** at a constant value for constant v_{GS}





Review of MOSFETs- Linear Region

 

 Review of MOSFETs: DC load line of n-MOSFET



Review of MOSFETs

  


Relation between V_{DS} & V_{GS}


Case	V_T	Channel condition
Linear region	$V_{DS} < V_{GS} - V_T$	Continuous inversion from source to drain
Pinch-off onset	$V_{DS} = V_{GS} - V_T$	Channel just disappears at drain end
Saturation	$V_{DS} > V_{GS} - V_T$	Pinch-off near drain, depletion region forms, current saturates

Review of MOSFETs

I_D - V_{DS} curves for various V_{GS} :

 


$$\beta = \mu C_{ox} \frac{W}{L}$$

 


$$I_D = \begin{cases} 0 & V_{gs} < V_t \quad \text{cutoff} \\ \beta \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds} & V_{ds} < V_{dsat} \quad \text{linear} \\ \frac{\beta}{2} (V_{gs} - V_t)^2 & V_{ds} > V_{dsat} \quad \text{saturation} \end{cases}$$

Review of MOSFETs: DC load line of n-MOSFET


I_D - V_{DS} curves for various V_{GS} :

 


Transfer characteristics:

 

 
Review of MOSFETs: DC load line of n-MOSFET




I_D - V_{DS} curves for various V_{GS} :

 

 Review of MOSFETs: DC load line of n-MOSFET




Load Line (Ckt Theory)

 

Review of MOSFETs

P-Channel MOSFETs


 
- Voltage polarities and doping types reversed relative to NMOS
 - ▣ N-type substrate
 - ▣ P⁺ drain and source
 - ▣ Negative threshold voltage: $V_{tp} < 0$
 - ▣ Negative overdrive voltage: $v_{OV} = v_{GS} - V_{tp} < 0$
 - ▣ Channel induced for $v_{GS} \leq V_{tp}$
 - ▣ Substrate connected to source or most positive circuit voltage




Review of MOSFETs

P-Channel MOSFETs

  - Voltage polarities and doping types reversed relative to NMOS
 - ▣ N-type substrate
 - ▣ P⁺ drain and source
 - ▣ Negative threshold voltage: $V_{tp} < 0$
 - ▣ Negative overdrive voltage: $v_{OV} = v_{GS} - V_{tp} < 0$
 - ▣ Channel induced for $v_{GS} \leq V_{tp}$
 - ▣ Substrate connected to source or most positive circuit voltage




(b) p-channel MOSFET

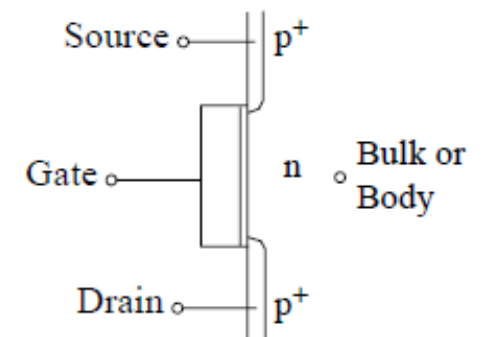


Review of MOSFETs

n-channel MOS
Transistor

 


p-channel MOS
Transistor

 

MOSFET type	$V_{GS} = +ve$	$V_{GS} = 0$	$V_{GS} = -ve$
N-Channel	ON	OFF	OFF
P-Channel	OFF	OFF	ON


MOSFET: Threshold Voltage (V_{th})

 - The voltage needed on the Gate terminal of the MOSFET to form a thin channel beneath the gate electrode (between Source & Drain terminals).
- The current can flow between S and D terminals through the channel.
- So threshold voltage is the voltage needed to turn on the device.
- As the MOSFET is voltage controlled current source, the output current will depend on the gate voltage applied.




MOSFET: Threshold Voltage (V_{th})

 - Lower V_{th} :
 - Faster in timing
 - Higher subthreshold current
- Higher V_{th} :
 - Less leakage
 - Higher delay
- V_{th} scales with MOSFET scaling




CMOS circuit

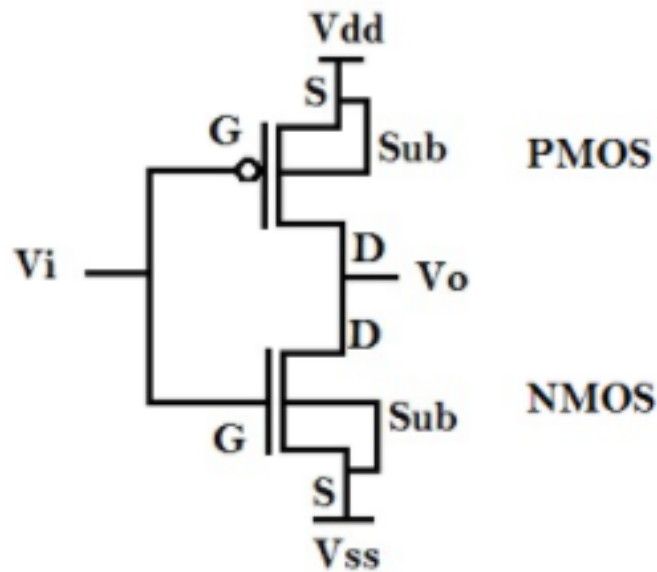




G = Gate Terminal
S = Source Terminal
D = Drain Terminal
Sub = Substrate Terminal

CMOS


 
- Complementary MOS or **CMOS**
 - ▣ Both NMOS and PMOS fabricated on the same chip
- P-type substrate
- PMOS devices fabricated in ***n wells***
- Most modern MOS chips are fabricated using CMOS technology




CMOS circuit

  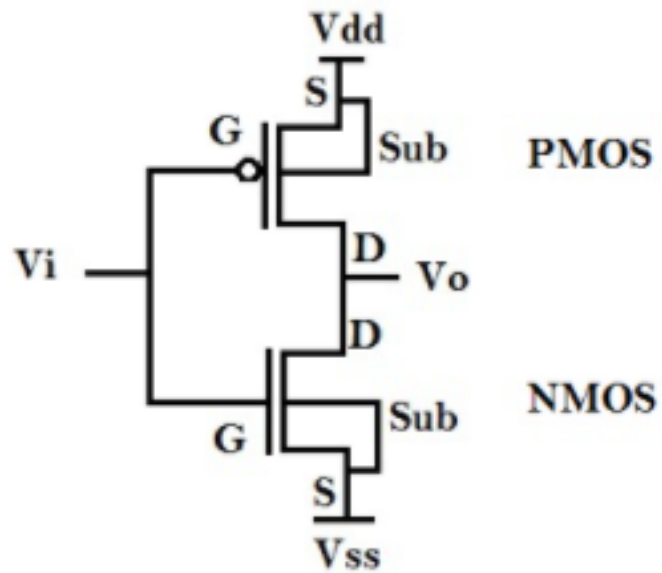



CMOS circuit

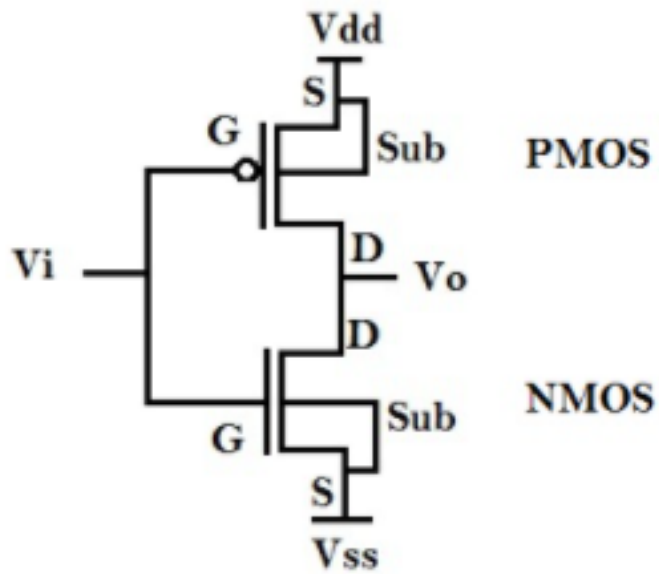 


CMOS Inverter Operation Principle

 



CMOS circuit

 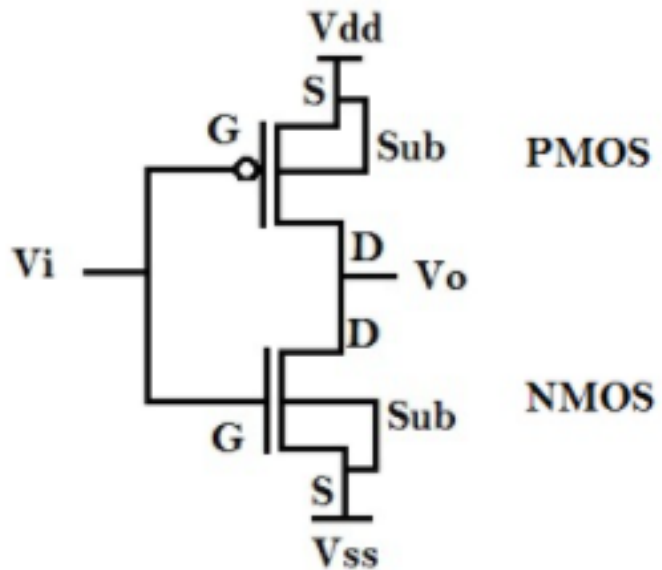


The Ideal Inverter

 



CMOS circuit

  



CMOS inverter transfer function

 



CMOS circuit

 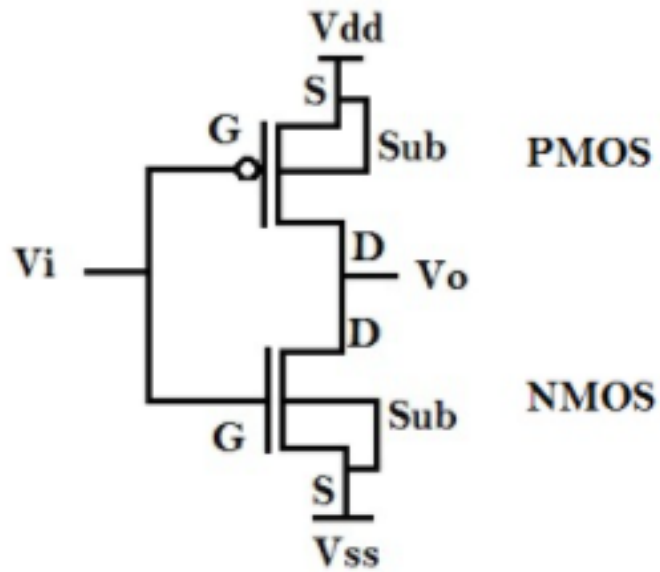


The Realistic Inverter

  

CMOS circuit

  

A CMOS inverter

 


Region	Condition	p-device	n-device	Output
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff	$V_{out} = V_{DD}$
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated	$V_{out} > V_{DD}/2$
C	$V_{in} = V_{DD}/2$	saturated	saturated	V_{out} drops sharply
D	$V_{DD}/2 < V_{in} \leq V_{DD} - V_{tp} $	saturated	linear	$V_{out} < V_{DD}/2$
E	$V_{in} > V_{DD} - V_{tp} $	cutoff	linear	$V_{out} = 0$


CMOS circuit

If $\beta_p / \beta_n \neq 1$, switching point will move from $V_{DD}/2$

$$\beta = \mu C_{ox} \frac{W}{L}$$

 


 
- $\beta_p > \beta_n$
HIGH SKEWED inverter
 $V_{in} = \frac{V_{DD}}{2} \rightarrow V_{out} > \frac{V_{DD}}{2}$
- $\beta_p < \beta_n$
LOW SKEWED inverter
 $V_{in} = \frac{V_{DD}}{2} \rightarrow V_{out} < \frac{V_{DD}}{2}$




CMOS circuit

CMOS Inverter (= NOT gate)


Table 1.1 Inverter truth table	
A	Y
0	1
1	0

  

CMOS circuit

 


INV

 

NAND



NOR

 


AND




OR

CMOS Logic NAND


Table 1.2 NAND gate truth table				
A	B	pull-down network	pull-up network	Y
0	0	OFF	ON	1
0	1	OFF	ON	1
1	0	OFF	ON	1
1	1	ON	OFF	0

 

$$Y = \overline{A \bullet B}$$

 


AND Gate

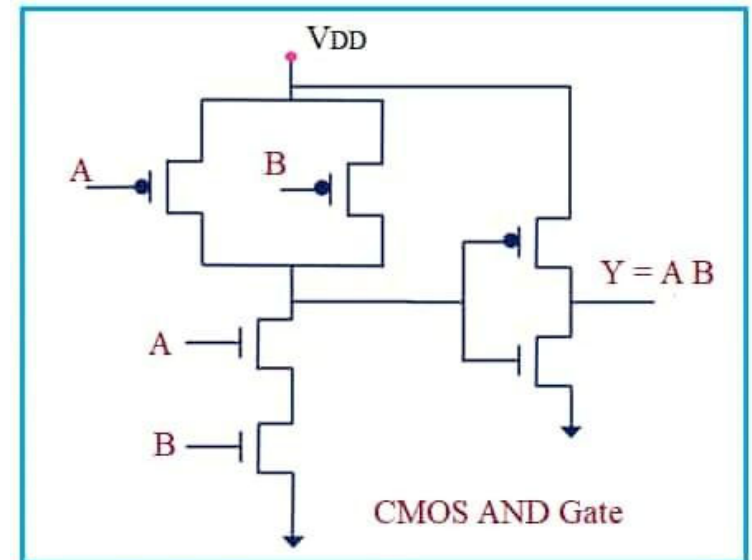


CMOS circuit

NOR Gate

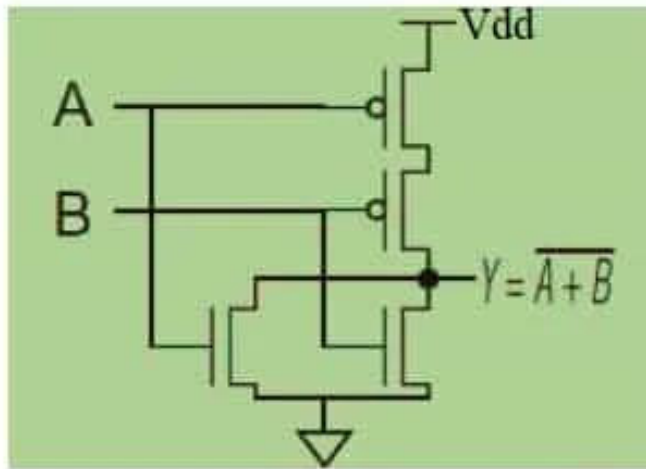

A	B	A NOR B
0	0	1
0	1	0
1	0	0
1	1	0


OR Gate

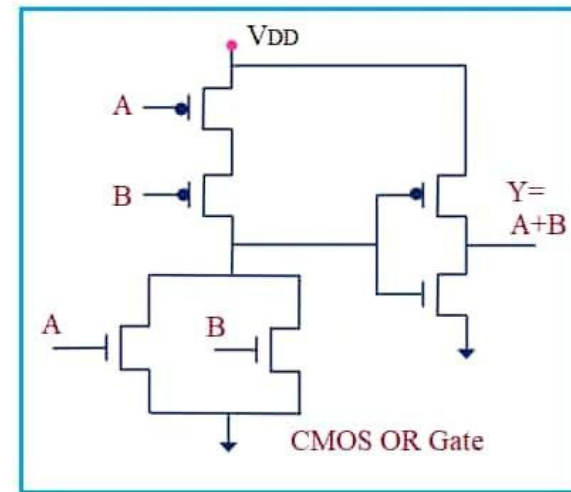

A	B	Output (A OR B)
0	0	0
0	1	1
1	0	1
1	1	1

CMOS circuit

Compound gates

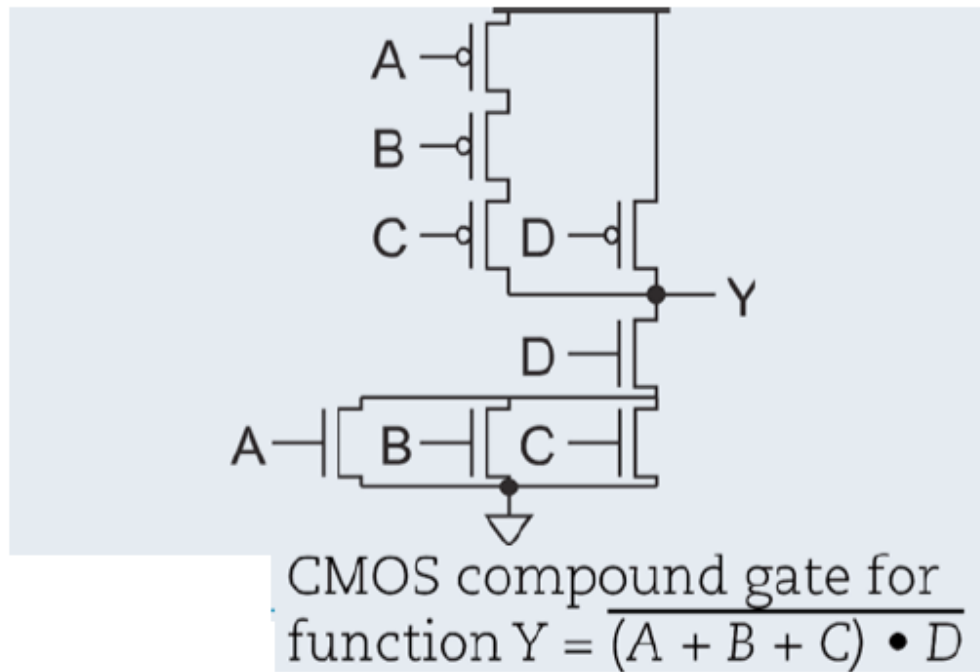

CMOS circuit: Noise Margin

- Noise margin is the ratio by which the signal exceeds the minimum acceptable amount.
- It explains up to what extent IC allows noise in the transmission of logic '0' and logic '1'.
- Logic '0' and '1' – represent the range of input values
- Hence, for error free digital signal transmission noise margin is required

CMOS circuit: Noise Margin

- **Noise margin** refers to how much unwanted noise (disturbance in voltage levels) a circuit can tolerate without misinterpreting logic levels. It essentially defines the safety “buffer” between valid logic-0 and logic-1 signals.
- Noise margin is critical in digital IC design because it ensures reliable operation in the presence of crosstalk, supply fluctuations, or electromagnetic interference.
- Higher V_{DD} gives bigger absolute noise margins, but modern technology scales V_{DD} down, so circuit design must ensure sufficient margins.


CMOS circuit: Noise Margin

- Noise margin is the ratio by which the signal exceeds the minimum acceptable amount.
- It explains up to what extent IC allows noise in the transmission of logic '0' and logic '1'.
- Logic '0' and '1' – represent the range of input values
- Hence, for error free digital signal transmission noise margin is required




CMOS circuit: Noise Margin

 - Noise margin is the ratio by which the signal exceeds the minimum acceptable amount.
- It explains up to what extent IC allows noise in the transmission of logic '0' and logic '1'.
- Logic '0' and '1' – represent the range of input values
- Hence, for error free digital signal transmission noise margin is required




CMOS circuit: Noise Margin

 


$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$

CMOS inverter transfer function

 

CMOS circuit: Noise Margin

 

$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$

CMOS circuit: Noise Margin

